

QUIZEN – 10P01 – Electricity

<i>Learning Level 1</i>	<i>Learning Level 2</i>	<i>Learning Level 3</i>
Q - Remembering (knowledge-based questions) U - Understanding (comprehension-based questions)	I - Applying (application-based questions) Z - Analyzing (analysis-based questions)	E - Evaluating (evaluation-based questions) N - Creating (creation-based questions)

Learning Level 1

Q1: Define resistance and give its unit.

Q2: State Ohm's law and explain its significance.

Q3: What is the potential difference across a resistance of $10\ \Omega$ if a current of $2\ \text{A}$ flows through it?

Q4: What is the resistance of a wire if a current of $2\ \text{A}$ flows through it when a potential difference of $4\ \text{V}$ is applied across it?

Q5: What is the current through a $5\ \Omega$ resistor if a potential difference of $20\ \text{V}$ is applied across it?

Learning Level 2

Q1: Two resistors of resistance $4\ \Omega$ and $6\ \Omega$ are connected in series. Calculate the equivalent resistance of the combination.

Q2: Two resistors of resistance $3\ \Omega$ and $9\ \Omega$ are connected in parallel. Calculate the equivalent resistance of the combination.

Q3: State Kirchhoff's first law and second law. Explain how they are used in solving problems related to electrical circuits.

Q4: What is the power dissipated in a resistor of $5\ \Omega$ when a current of $2\ \text{A}$ flows through it?

Q5: Two resistors of resistance $10\ \Omega$ and $20\ \Omega$ are connected in series. Calculate the voltage drop across the $20\ \Omega$ resistor when a potential difference of $120\ \text{V}$ is applied across the combination.

Learning Level 3

Q1: Explain why the resistance of a conductor increases with its temperature.

Q2: A bulb rated at 100 W, 220 V is connected across a 110 V supply. What will be the power consumed by the bulb? Explain.

Q3: A current of 2 A flows through a $10\ \Omega$ resistor for 5 minutes. Calculate the amount of electrical energy consumed by the resistor.

Q4: What is an electric fuse? How does it work?

Q5: Design a circuit using a 12 V battery and three resistors such that the current passing through the resistors is 0.5 A

create curve